



# **ECE232: Hardware Organization and Design**

## Lecture 8: Multiplication

Adapted from *Computer Organization and Design*, Patterson & Hennessy, UCB

# MULTIPLY (unsigned)

---

- Paper and pencil example (unsigned):


<b>Multiplicand</b>	1000
<b>Multiplier</b>	<u>1001</u>
	1000
	0000
	0000
	<u>1000</u>
<b>Product</b>	1001000

- $m$  bits  $\times$   $n$  bits =  $m+n$  bit product
- Binary makes it easy:
  - 0  $\rightarrow$  place 0 ( 0  $\times$  multiplicand)
  - 1  $\rightarrow$  place a copy ( 1  $\times$  multiplicand)
- 3 versions of multiply hardware & algorithm:
  - successive refinement
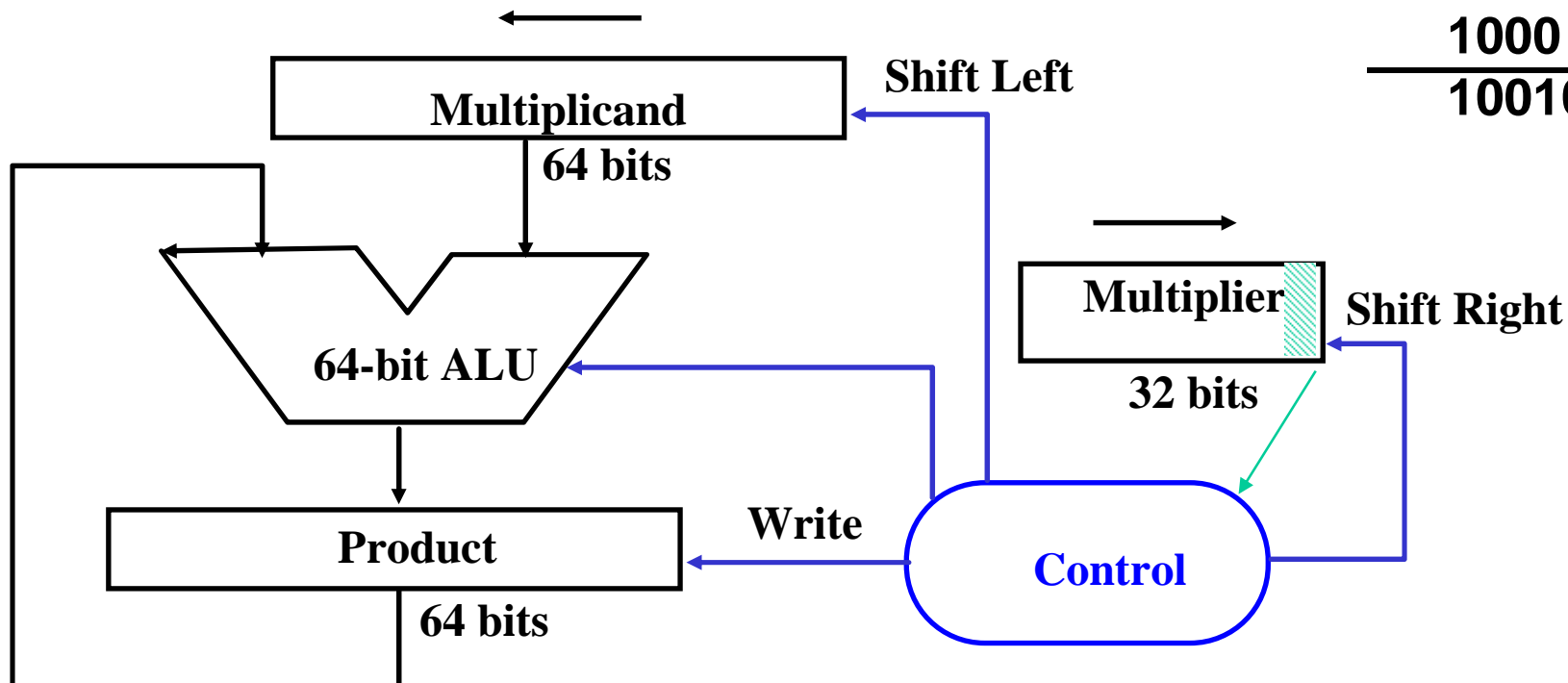
# Unsigned shift-add multiplier (version 1)

- 64-bit Multiplicand reg, 64-bit ALU,  
64-bit Product reg,  
32-bit multiplier reg


```
      1000
      1001
      ----
      1000
    0000
    0000
    1000
    ----
   1001000
```



**Multiplier = datapath + control**

# Multiply Algorithm - Version 1: Control

Product	Multiplier	Multiplicand
0000 0000	0011	0000 0010
0000 0010	0001	0000 0100
0000 0110	0000	0000 1000
0000 0110		

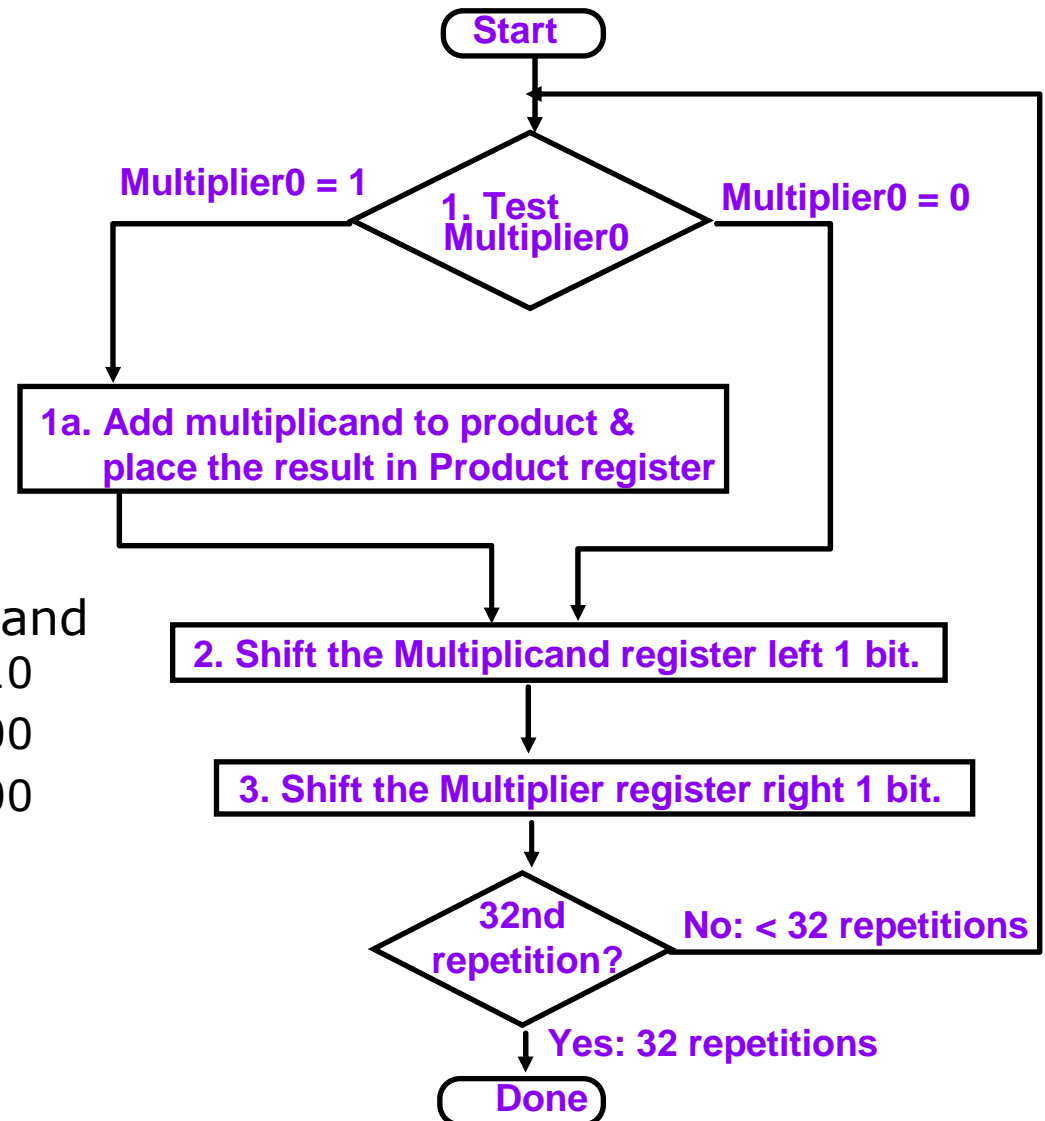

# Observations on Multiply Version 1


---

- 1 cycle per step  $\rightarrow 32 \times 3 = \sim 100$  cycles per multiply. However, One cycle per iteration can be saved by shifting multiplier and multiplicand in one cycle  $\rightarrow 32 \times 2$
- 50% of the bits in multiplicand are 0  
 $\rightarrow$  64-bit adder is wasted
- 0s inserted in right of multiplicand as shifted to the left  $\rightarrow$  least significant bits of product never changed once formed
- Instead of shifting multiplicand to left, shift product to the right


$$\begin{array}{r} 1001 \\ 1010 \\ \hline 0000 \\ 1001 \\ 0000 \\ 1001 \\ \hline 10100010 \end{array}$$
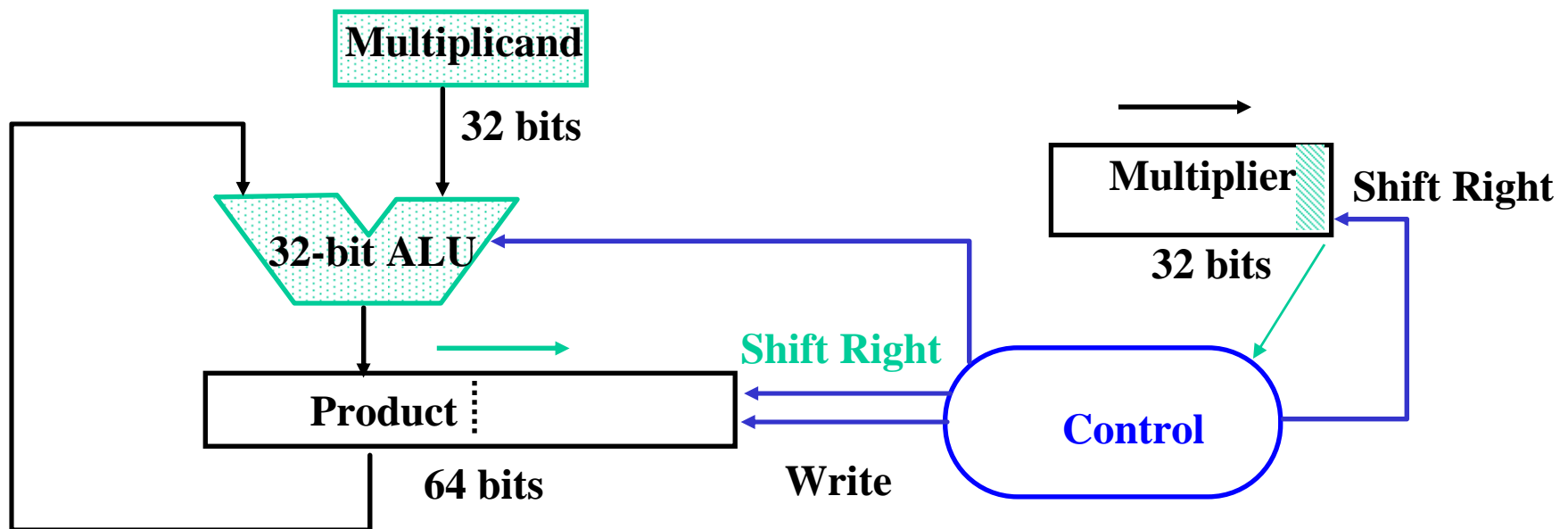
# Multiply Hardware - Version 2

- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg



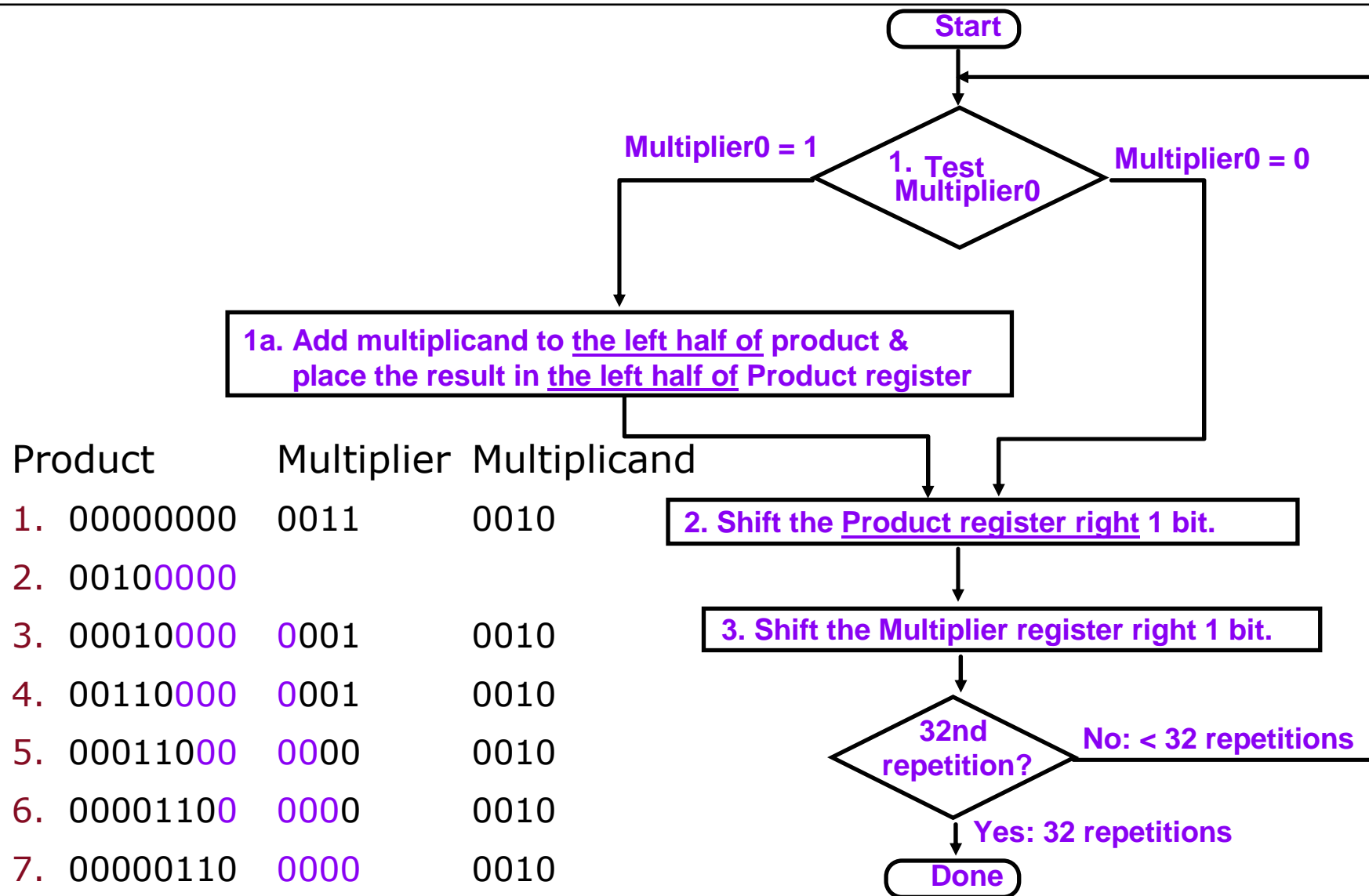
# Multiply Algorithm - Version 2: Control



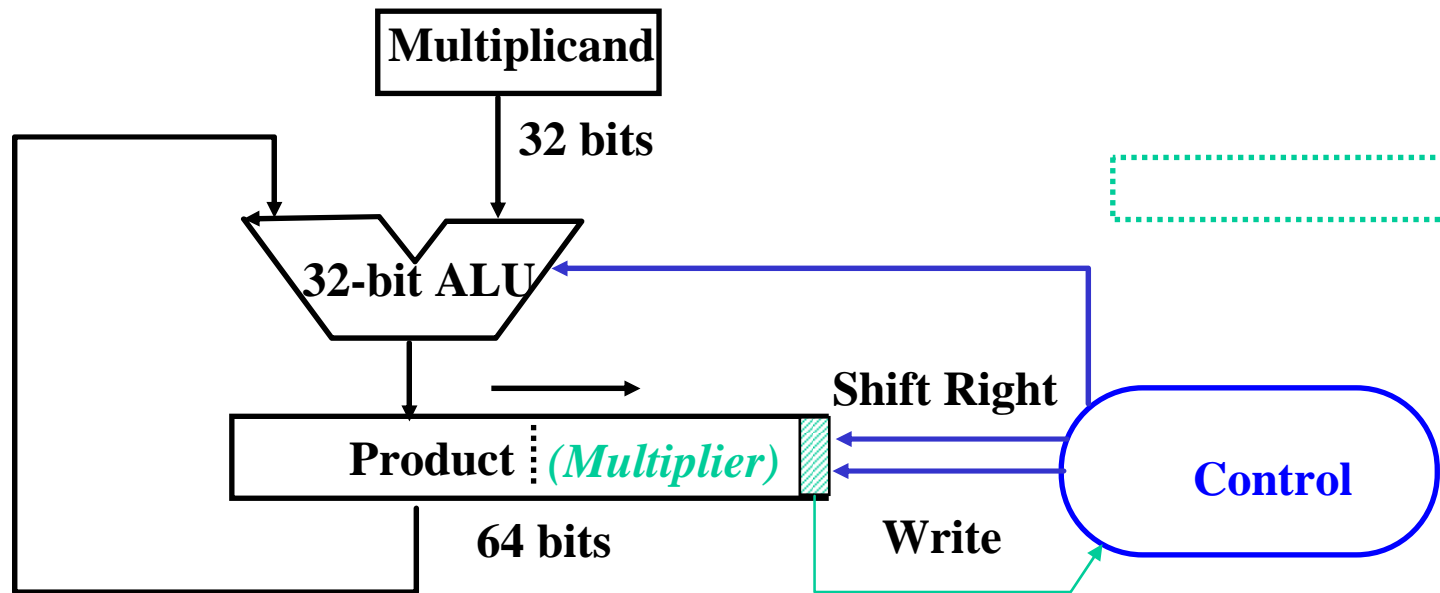
# Multiply Hardware - Version 3

- Product register wastes space that exactly matches size of multiplier
  - combine Multiplier register and Product register
- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)




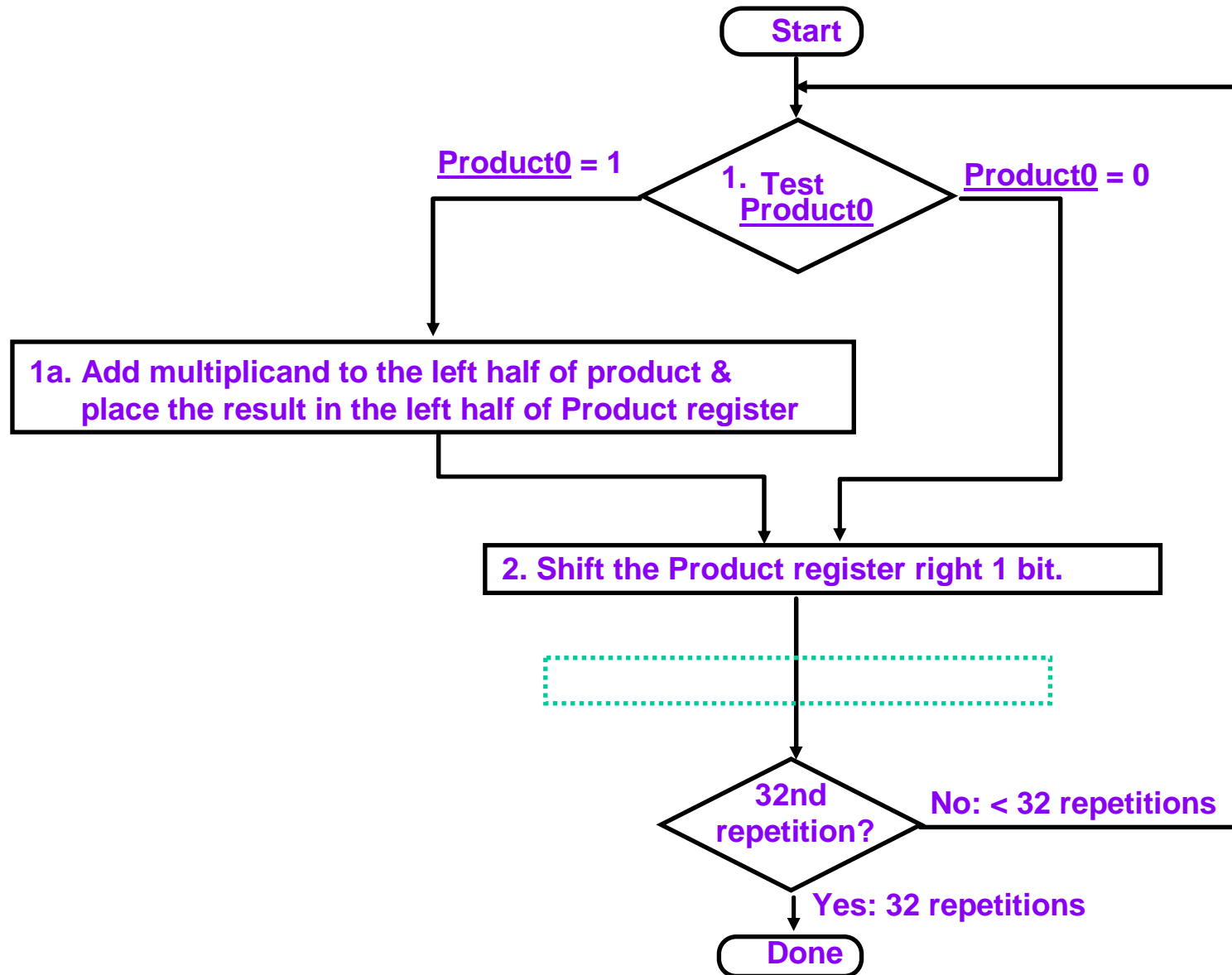
# Multiply Algorithm - Version 3: Control




# Observations on Multiply Version 3

- 2 steps per bit because Multiplier & Product combined
- How can you make it faster?
- What about signed multiplication?
  - trivial solution: make both positive & complement product if one of operands is negative (leave out the sign bit, run for 31 steps)
  - apply definition of 2's complement
    - need to sign-extend partial products

$A$		1	0	1	1					$-5$
$X$	$\times$	0	0	1	1					$3$
$P^{(0)} = 0$		0	0	0	0					
$x_0 = 1 \Rightarrow \text{Add } A$	$+$	1	0	1	1					
		1	0	1	1					
Shift		1	1	0	1	$1$				
$x_1 = 1 \Rightarrow \text{Add } A$	$+$	1	0	1	1					
		1	0	0	0	$1$				
Shift		1	1	0	0	$0 \quad 1$				
$x_2 = 0 \Rightarrow \text{Shift only}$		1	1	1	0	$0 \quad 0 \quad 1$				$-15$
 
# Faster Multiplier

- Uses multiple adders
  - Cost/performance tradeoff



- Can be pipelined
  - Several multiplication performed in parallel

# MIPS Multiplication

---

- Two 32-bit registers for product
  - HI: most-significant 32 bits
  - LO: least-significant 32-bits
- Instructions
  - `mult rs, rt` / `multu rs, rt`
    - 64-bit product in HI/LO
  - `mfhi rd` / `mflo rd`
    - Move from HI/LO to rd
    - Can test HI value to see if product overflows 32 bits
  - `mul rd, rs, rt`
    - Least-significant 32 bits of product -> rd

# Summary

---

- Multiplication in computers generally takes longer than addition
- Lots of creative solutions for multiplier design
  - Minimize hardware
  - Best possible performance
- Note format of MIPS multiplication instructions
- Division similar